
EEE 111 Lab – MultiSim Assignment


Net Names (Node Number) must be visible on your MultiSim circuit.
Write your Name, ID, Group Number as Text beside your circuit diagram.
Create your assignment on a DOC/Word file, convert it in a PDF, then upload.

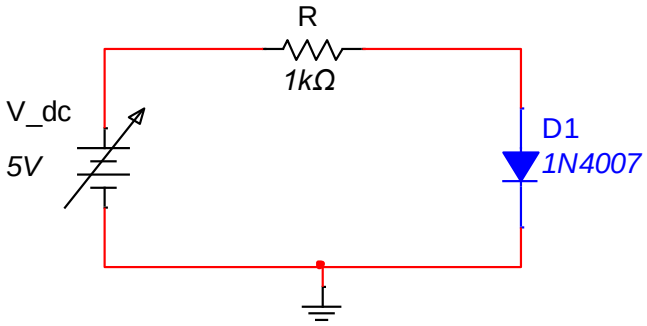1. Design the following circuit. Then, using Interactive simulation (using multimeter), find out the following data and fill up the table.



V_{DC}	V_R	V_D	I_D
0.2 V			
0.4 V			
0.6 V			
0.8 V			
1.0 V			

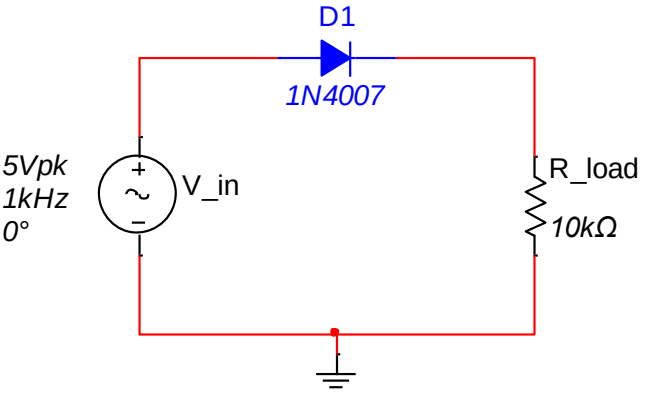2. Design the following half-wave rectifier circuit. Then, using transient analysis, find out the input and output graph.




You'll find AC Voltage source in Source > Signal_Voltage_Source > AC_Voltage

For Transient analysis, set

- Start time = 1.000 sec
- Stop time = 1.005 sec
- Select maximum time stem
- On output tab, select appropriate variables to see input and output graph.

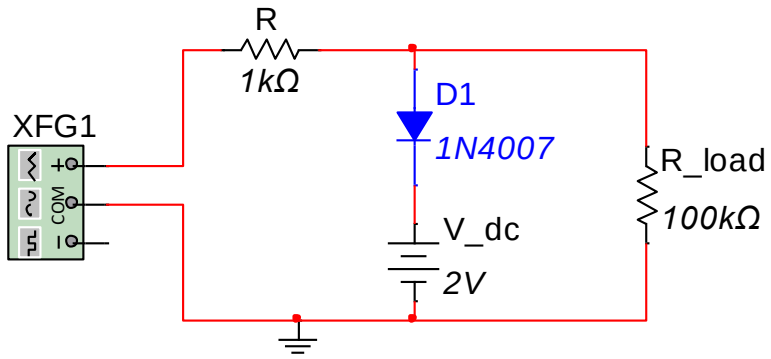
3. Design the following clipper circuit. Set AC Input as $5V_{pk}$ – 1 kHz – Triangle wave. Then, using transient analysis, find out the input and output graph.



For Transient analysis, set

- Start time = 1.000 sec
- Stop time = 1.005 sec
- Select maximum time stem
- On output tab, select appropriate variables to see input and output graph.

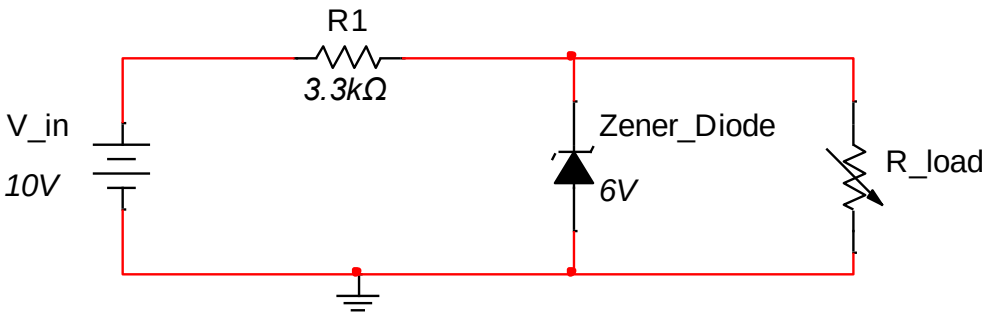4. Design the following circuit. Then, using Interactive simulation (using multimeter), find out the following data and fill up the table.



R_{load}	V_{R1}	V_{R_load}	I_{R_load}
1 kΩ			
3.3 kΩ			
10 kΩ			
33 kΩ			
100 kΩ			